

## CSE 3203 CT 4 Assignment

Roll No: 1903113

**Instruction: Covert this doc to PDF while uploading.**

### Assignment Problem:

Build CPU based on following requirements:

1. Word Size of CPU = 3
2. ALU Operations = NOT, ADD, ROL
3. Register Number = 6
4. Size of RAM = 7
5. Word size of ISA and RAM = 17
6. CPU Instructions = Register Mode, Immediate Mode, Branching (JMP,JE)

### Solution:

**Video Link (Youtube Video Link/Google Drive Link with Necessary Drive Permissions):**

[https://drive.google.com/file/d/1hEJckZhHeKJ9AnfUy1mZLIY4GcYSTy1k/view?usp=drive\\_link](https://drive.google.com/file/d/1hEJckZhHeKJ9AnfUy1mZLIY4GcYSTy1k/view?usp=drive_link)

### Simulator Design:

1. ALU Circuit (Show all circuits except FA circuit)(Marks 5):

Check List:

Have you added all circuits of ALU from FA to ALU Operations Circuits (ADD, XOR, SHL etc.) to Top Level ALU Circuit?	YES
--	-----

<b>NB: Failing to add any required circuits will cause point penalty (1-2 Marks)</b>	
--	--

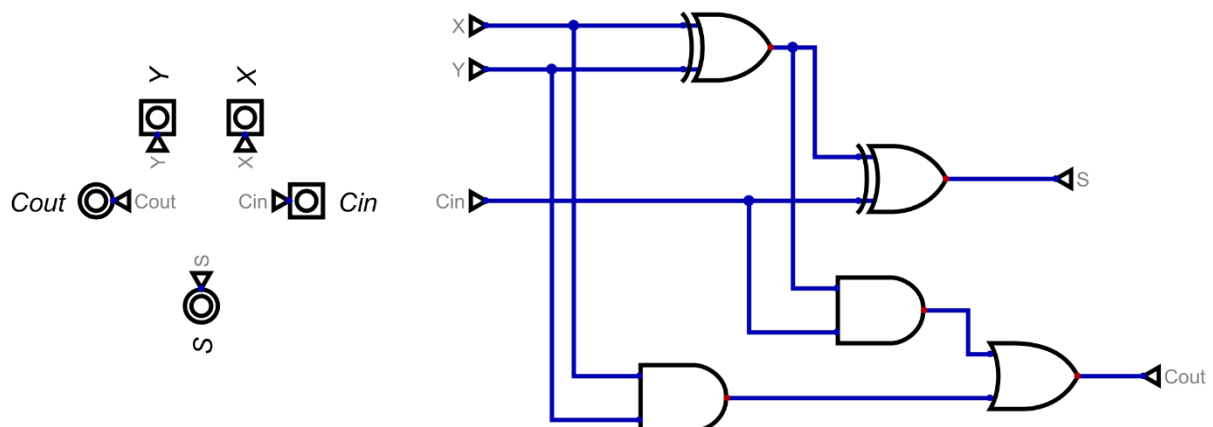


Fig 1.1: Full Adder Circuit

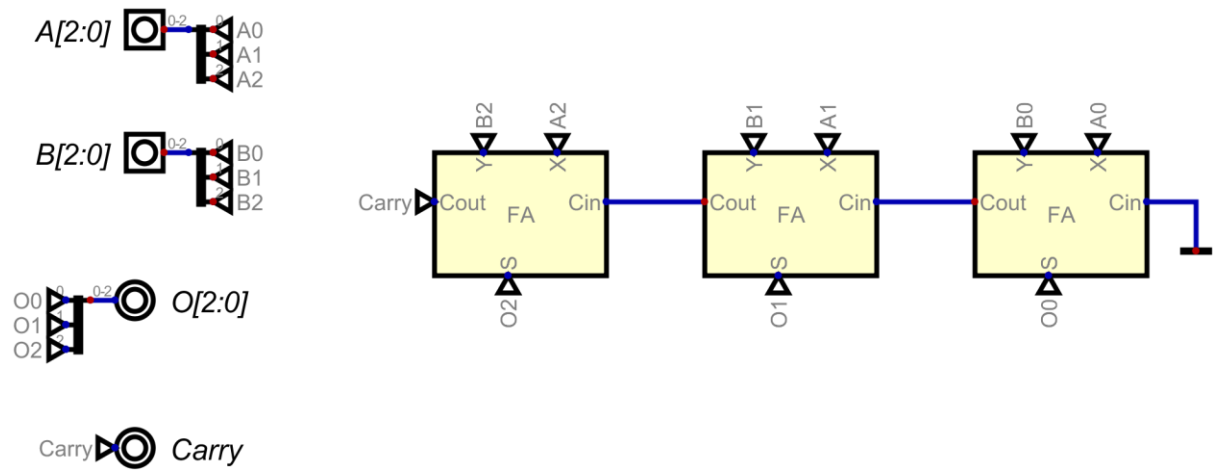


Fig 1.2: 3 Bit Adder Circuit

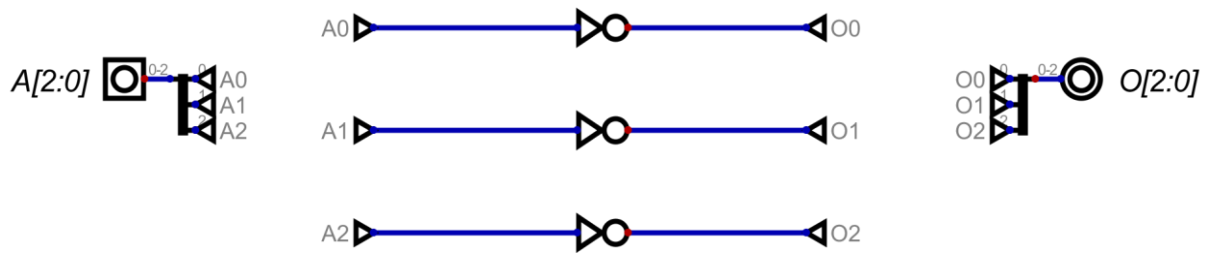


Fig 1.3: 3 Bit Not Circuit

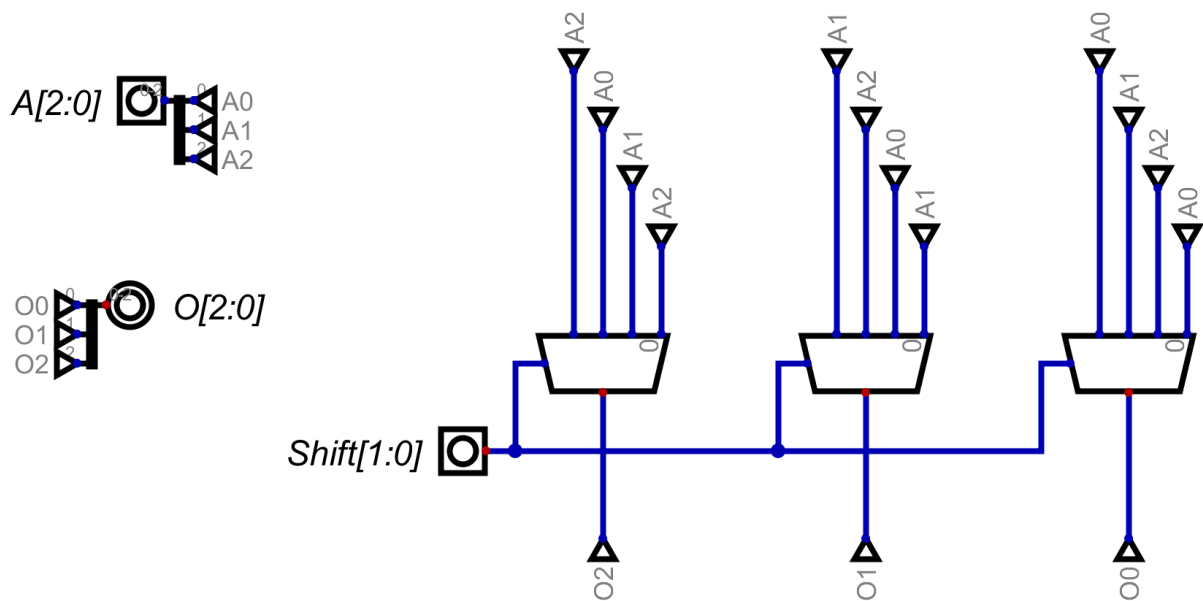


Fig 1.4: 3 Bit Rotate Left Circuit

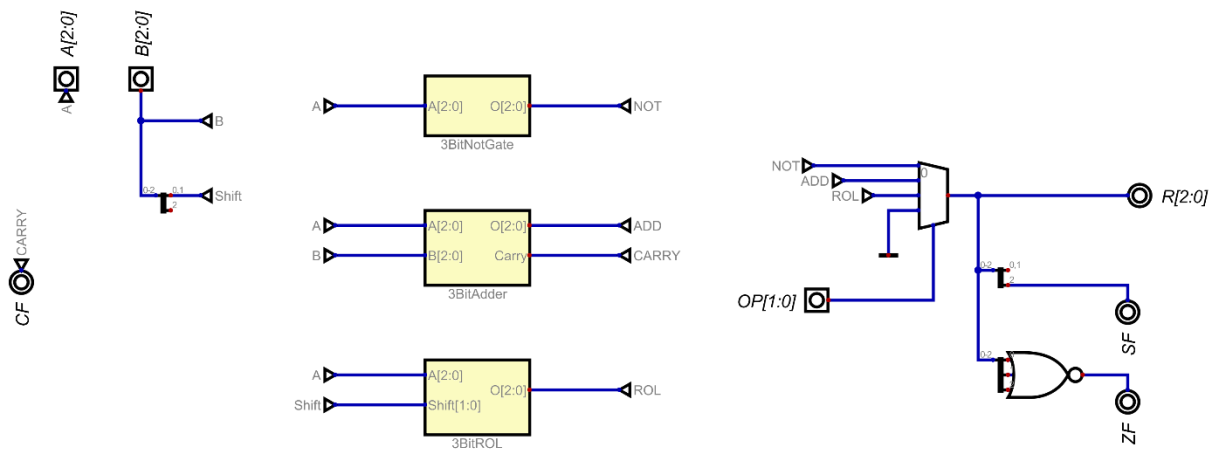


Fig 1.5: 3 Bit ALU Circuit

## 2. Register Set Circuit (Top to Bottom all circuits)(5 Marks):

### Check List:

Have you added all circuits of Register Set from 1 bit Register to n bit Register to Top Level Register Set Circuit.?	YES
<b>NB: Failing to add any required circuits will cause point penalty (1-2 Marks)</b>	


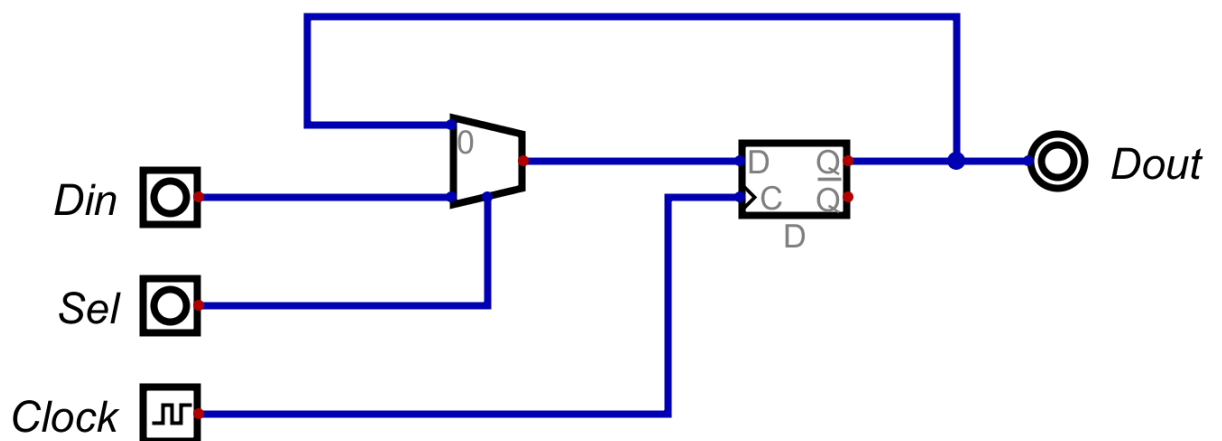
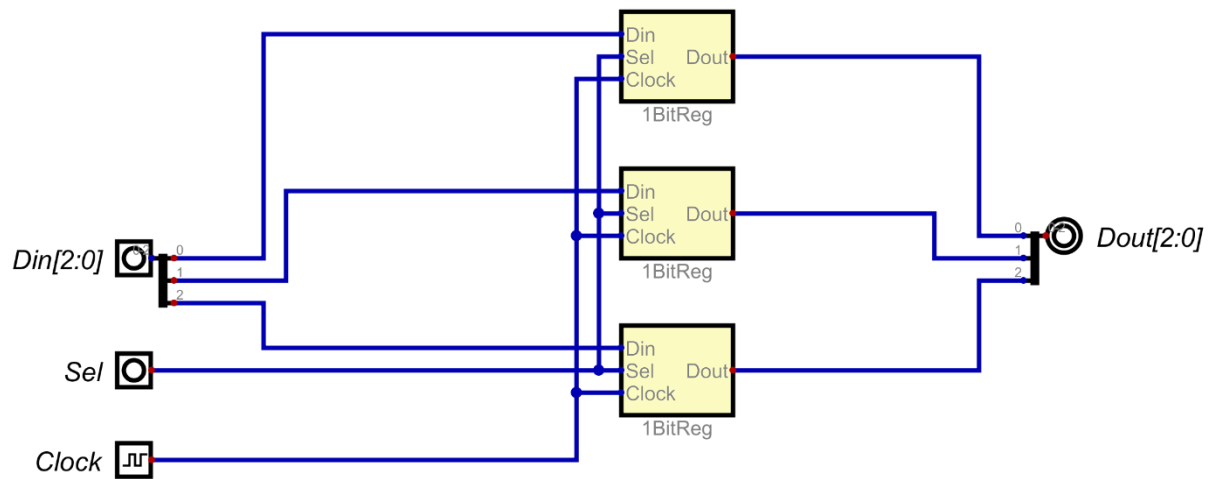


Fig 2.1: 1 Bit Register

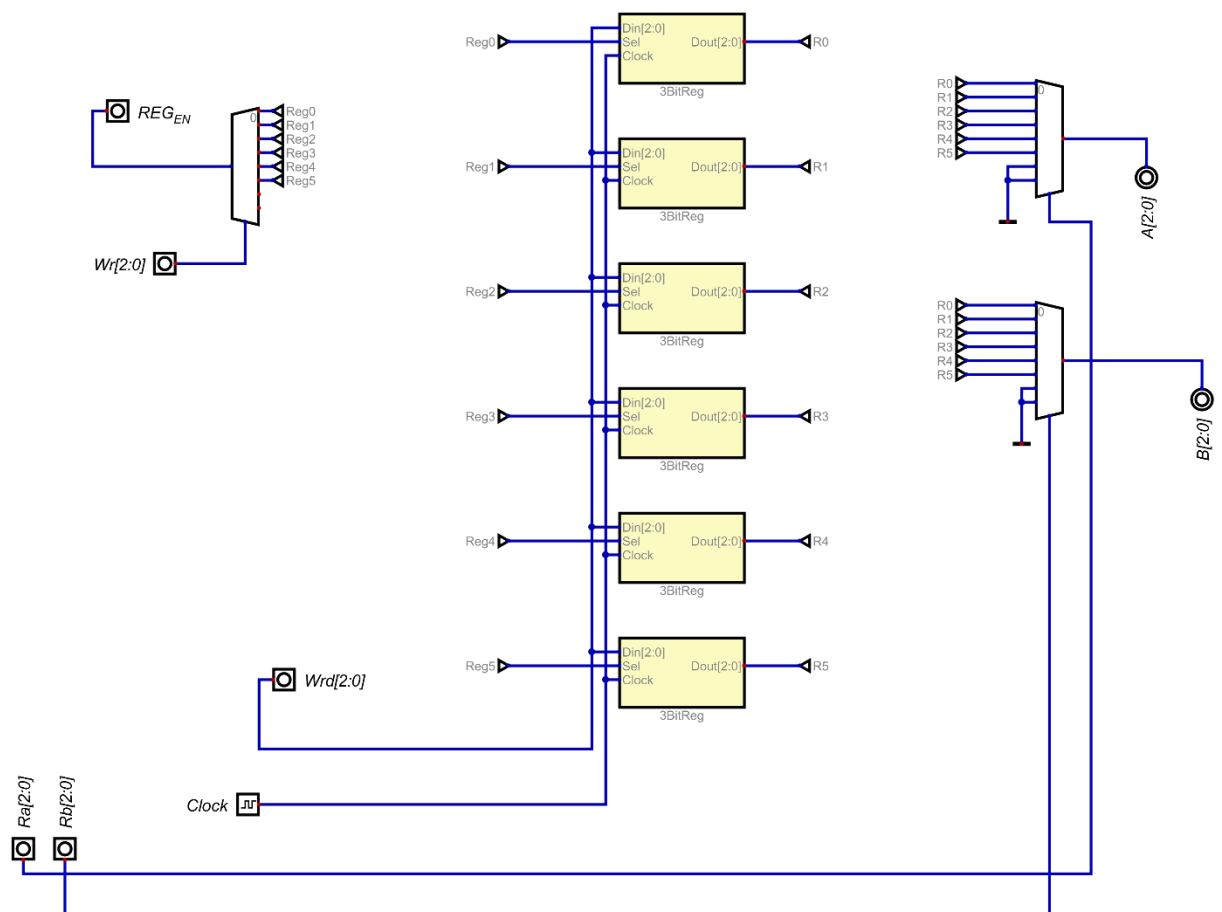

**Fig 2.2: 3 Bit Register**

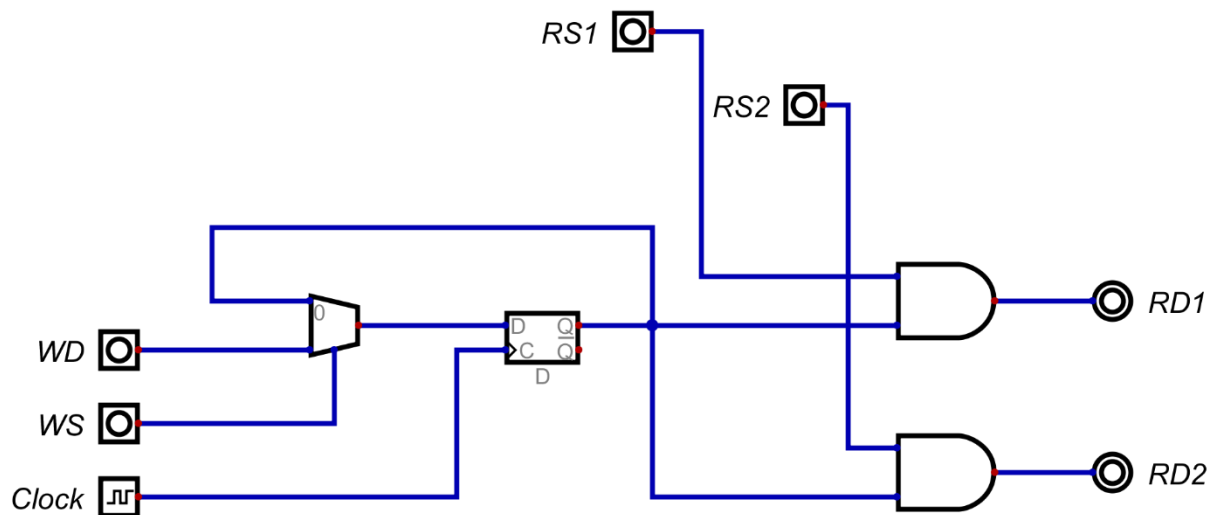


**Fig 2.3: 6 x 3 Bit Register Set**


**3. RAM Circuit (Top to Bottom all circuits)(5 Marks):**

### Check List:

Have you added all circuits of RAM from 1x1 RAM to 1xN RAM to MxN RAM?	YES
<b>NB: Failing to add any required circuits will cause point penalty (1-2 Marks)</b>	



**Fig 3.1: 1 x 1 RAM**

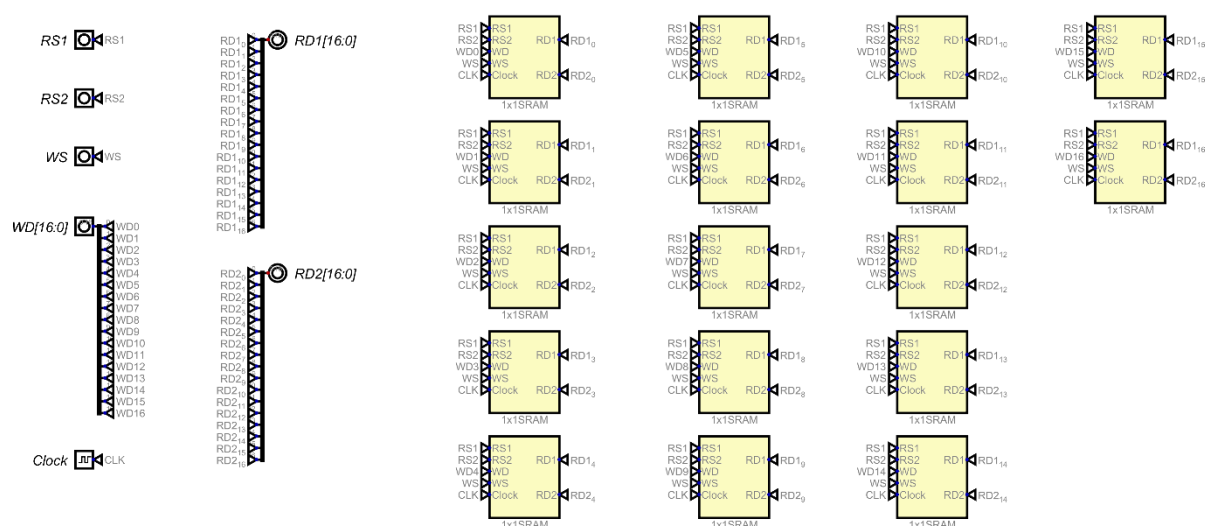

**Fig 3.2: 1 x 17 RAM**

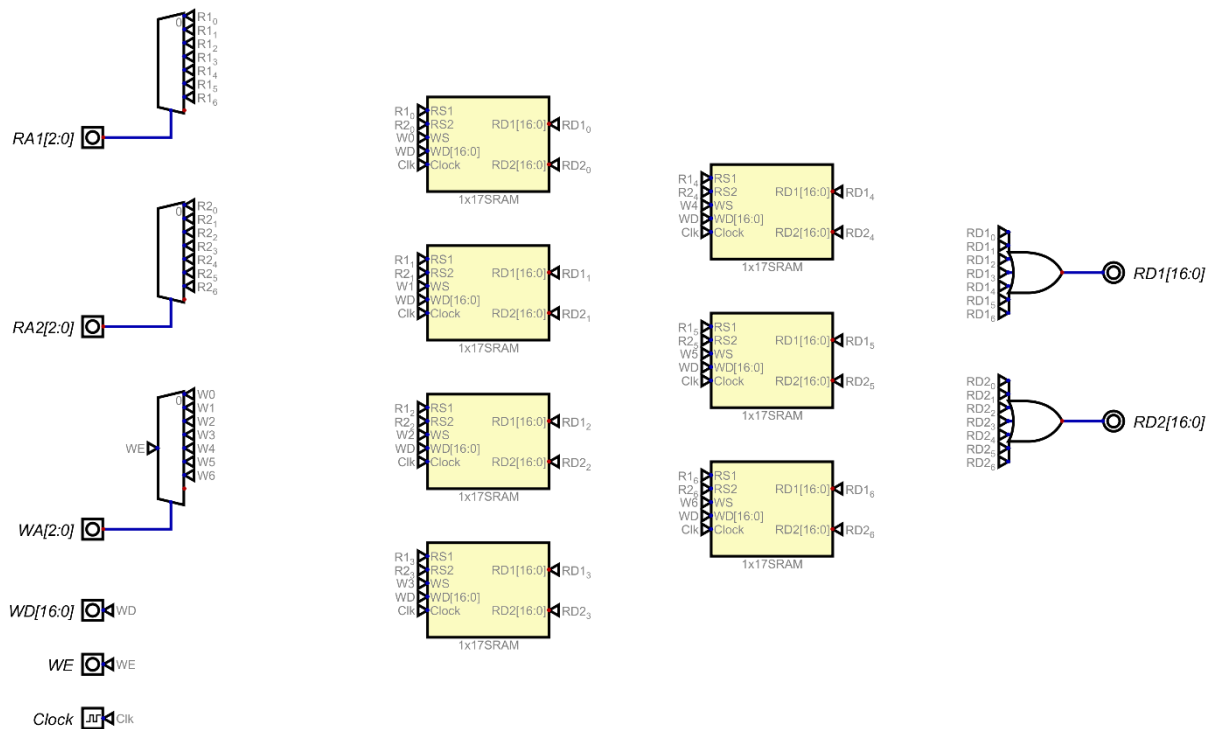


Fig 3.3: 7 x 17 RAM

#### 4. a) ISA (2 Marks)

##### Check List:

Have you added all ISA of CPU along with its sample machine code to be run on CPU?

YES

**NB: Failing to add any required ISA or sample code will cause point penalty (1-2 Marks)**

##### ISA (Register Mode):

Opcode (4 bit)		Register 1	Register 2	Unused
2 bits	2 bits	3 bits	3 bits	7 bits
Types of instruction	Operations (ALU selection lines)	Ra (000-101)	Rb (000-101)	XXXXXXX
00	NOT – 00 ADD – 01 ROL – 10			

**ISA (Immediate Mode):**

Opcode (4 bit)		Register 1	Immediate value	Unused
2 bits	2 bits	3 bits	3 bits	7 bits
Types of instruction  01	Operations (ALU selection lines) NOT – 00 ADD – 01 ROL – 10	Ra (000-101)	Rb (000-111)	XXXXXXX

**ISA (Branching Mode):**

Opcode (4 bit)		Jump Label	Unused
2 bits	2 bits	3 bits	10 bits
Types of instruction  10	Operations (JUMP selection lines) JMP – 00 JE – 01	LABEL (000-110)	XXXXXXXXXX


**Sample Machine Code with assembly code in comments to be run on CPU (You will make a video running this machine code on CPU in order to prove that your CPU is working perfectly)**

Machine Code	Assembly Code
0101000011XXXXXXXX	ADD R0, 3
0101001010XXXXXXXX	ADD R1, 2
0001000001XXXXXXXX	JMP_TO_1: ADD R0, R1
1001010XXXXXXXXXX	JE JMP_TO_1
0110001010XXXXXXXX	JMP_TO_2: ROL R1,2
0000001XXXXXXXXXX	NOT R1
1000100XXXXXXXXXX	JMP JMP_TO_2


**b) CPU (Top to Bottom all circuits)(3 Marks):**

**Check List:**

Have you added all circuits of CPU from Program Counter to Control Unit to Top Level CPU Circuit with <b>Output Pins showing contents of ALU, Register Set, RAM etc. (Important for CPU Verification, Check Tutorial Videos for Details)?</b>	YES
Have you made a video running this sample machine code on the CPU (1 instruction at a time in a similar way shown in video) in order to prove that your CPU is working perfectly.	YES
<b>NB: Failing to add any required circuits will cause point penalty (1-2 Marks)</b> <b>NB: Failing to add video will cause point penalty from CPU segment (3 Marks)</b>	

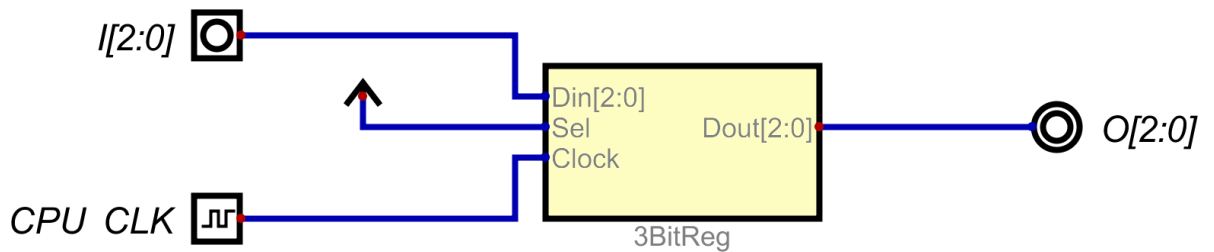

**Fig 4.1: 3 Bit Program Counter**

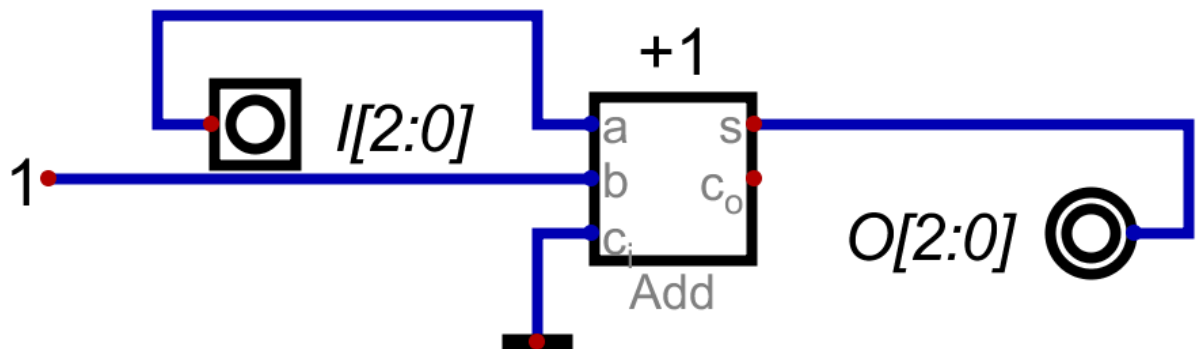

**Fig 4.2: 3 Bit Add One Circuit**



